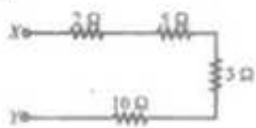


# PAGE 4

## Exercise

1. Calculate the total resistance for each case


a)



$$R_T = 2 + 5 + 3 + 10$$

$$= \underline{20\Omega}$$


b)

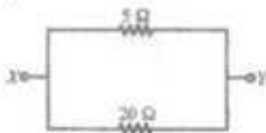

$$\frac{1}{R_T} = \frac{1}{5} + \frac{1}{20} = \frac{1}{4}$$

$$R_T = \underline{4\Omega}$$


c)

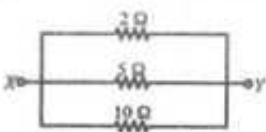

$$\frac{1}{R_T} = \frac{1}{2} + \frac{1}{5} + \frac{1}{10} = \frac{4}{5}$$

$$R_T = \underline{\frac{5}{4}\Omega}$$

d)

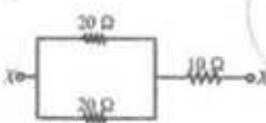

$$\frac{1}{R} = \frac{1}{20} + \frac{1}{30} = \frac{1}{10}$$

$$R = 10\Omega$$

$$R_T = 10 + 10 = \underline{20\Omega}$$

e)



$$R = 5 + 5 = 10\Omega$$

$$\frac{1}{R_T} = \frac{1}{10} + \frac{1}{5} = \frac{3}{10}$$

$$R_T = \underline{\frac{10}{3}\Omega}$$

f)



$$R = 5 + 5 = 10\Omega$$

$$R = 5 + 15 = 20\Omega$$

$$\frac{1}{R} = \frac{1}{10} + \frac{1}{20}$$


$$R = \frac{20}{3}\Omega$$

$$R_T = \frac{20}{3} + 8 = \underline{\frac{44}{3}\Omega}$$

# PAGE 5

2. For the circuit below find the missing value

a)

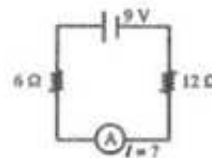


$$R_T = 6 + 12 = 18\Omega$$

$$V = IR$$

$$9 = I(18)$$

$$I = \underline{0.5A}$$

b)

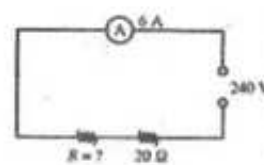


$$V = IR$$

$$240 = 6(R + 20)$$

$$40 = R + 20$$

$$R = \underline{20\Omega}$$

c)

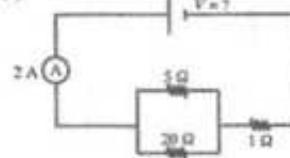


$$\frac{1}{R} = \frac{1}{5} + \frac{1}{20} = \frac{1}{4}$$

$$R = 4\Omega, R_T = 4 + 1 = 5\Omega$$

$$V = IR = 2(5) = \underline{10V}$$

d)

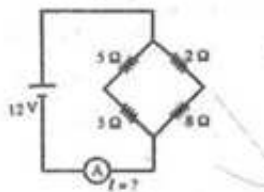


$$R = 5 + 5 = 10\Omega$$

$$R = 2 + 8 = 10\Omega$$

$$\frac{1}{R_T} = \frac{1}{10} + \frac{1}{10} = \frac{1}{5}$$

$$R_T = 5\Omega$$

(c)

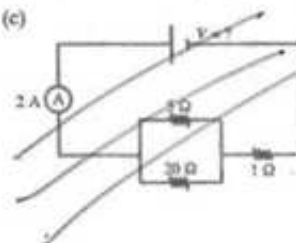


$$V = IR$$

$$12 = I(5)$$

$$I = \underline{2.4A}$$

# PAGE 6

3.

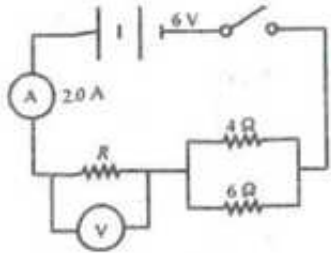

For the circuit above, calculate

- Total effective resistance
- Value of R
- The voltmeter reading


$$\begin{aligned} a) \quad V &= IR \\ 6 &= 2R \\ R_T &= 3\Omega \end{aligned}$$

$$\begin{aligned} b) \quad \frac{1}{R_T} &= \frac{1}{4} + \frac{1}{6} = \frac{5}{12} \\ R_T &= \frac{12}{5} = 2.4\Omega \end{aligned}$$

$$\begin{aligned} R + 2.4 &= 3\Omega \\ R &= 0.6\Omega \end{aligned}$$

$$\begin{aligned} c) \quad V &= IR \\ &= 2(0.6) = 1.2V \end{aligned}$$

4.

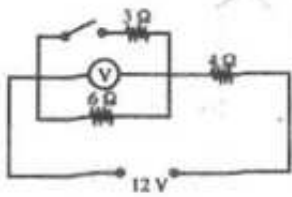

Calculate the voltmeter reading when

- The switch is ON
- The switch is OFF


$$a) \quad \frac{1}{R} = \frac{1}{3} + \frac{1}{6} = \frac{1}{2}$$

$$R = 2\Omega$$

$$\begin{aligned} V_{2\Omega} &= \left(\frac{2}{2+4}\right) \times 12 \\ &= 4V \end{aligned}$$

$$\begin{aligned} b) \quad V_{6\Omega} &= \left(\frac{6}{6+4}\right) \times 12 \\ &= 7.2V \end{aligned}$$

5.

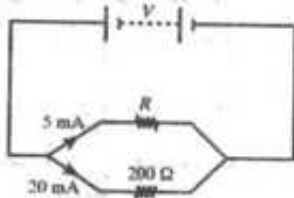


For the circuit above, calculate the value of R

$$\begin{aligned} V_R &= V_{200\Omega} \\ 5 \times 10^{-3} R &= (20 \times 10^{-3})(200) \\ R &= 800\Omega \end{aligned}$$

# PAGE 8

## Exercise

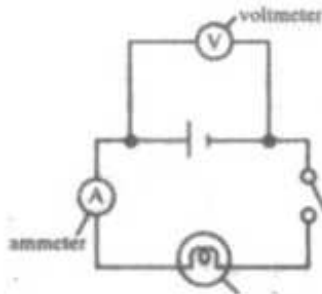

$$\begin{aligned} \mathcal{E} &= 1.5 \text{ V} \\ V_{\text{ext}} &= 1.35 \text{ V} \\ V_{\text{int}} &= 0.15 \text{ V} \\ V_{\text{int}} &= Ir \\ 0.15 &= 0.3r \\ r &= 0.05 \Omega \end{aligned}$$

1. Diagram above shown that when the switch is OFF, the voltmeter reading is 1.5 V. When the switch is ON, the voltmeter reading become 1.35 V and the ammeter show a 0.3A reading. Find the internal resistance for the cell

2. A dry cell with e.m.f 3.0 V and internal resistance 0.5  $\Omega$  is connected to a resistor R  $\Omega$ . If the current flow in the circuit is 0.4 A. Calculate

$$V_{\text{ext}} = IR$$

$$I = 0.4 \text{ A}$$

$$R = 7 \Omega$$


- a) potential difference at the resistor  
b) the value of R

$$\begin{aligned} \mathcal{E} &= V_{\text{ext}} + V_{\text{int}} \\ V_{\text{ext}} &= 3 - 0.4(0.5) \\ &= 2.8 \text{ V} \end{aligned}$$

3. A cell with internal resistance 2.0  $\Omega$ . Potential difference for the cell at the external terminal is 2.4 V when there is 0.3 A current flow. Calculate the e.m.f of the cell

$$\begin{aligned} r &= 2 \Omega, V_{\text{ext}} = 2.4 \text{ V} \\ I &= 0.3 \text{ A}, \mathcal{E} = V_{\text{ext}} + Ir \\ &= 2.4 + 0.3(2) \\ &= 3 \text{ V} \end{aligned}$$

- 4.

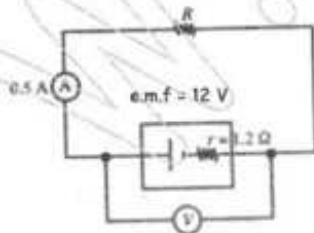

$$\begin{aligned} \mathcal{E} &= V_{\text{ext}} + V_{\text{int}} \\ V_{\text{ext}} &= 12 - 0.5(1.2) \\ &= 11.4 \text{ V} \end{aligned}$$


For the circuit above, calculate

- a) the voltmeter reading  
b) external resistance for the cell

$$\begin{aligned} V_{\text{ext}} &= IR \\ 11.4 &= 0.5R \end{aligned}$$

# PAGE 9

- 5.

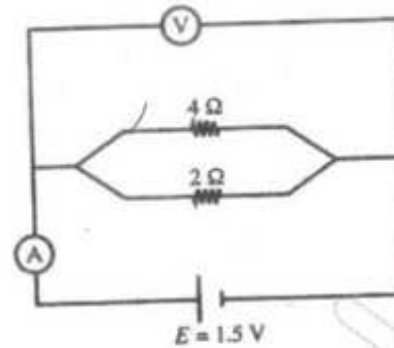

$$1) \frac{1}{R} = \frac{1}{4} + \frac{1}{2} = \frac{3}{4}$$

$$R = \frac{4}{3} \Omega$$

$$\mathcal{E} = I(R+r)$$

$$1.5 = I\left(\frac{4}{3} + 2\right)$$


$$I = 0.45 \text{ A}$$

$$\begin{aligned} \text{b) } V_{\text{ext}} &= \mathcal{E} - Ir \\ &= 1.5 - 0.45(2) \\ &= 0.6 \text{ V} \end{aligned}$$

A cell with e.m.f = 1.5 V is connected to the circuit as shown in the diagram above

- a) If the internal resistance of the cell is 2  $\Omega$ , calculate the current flow in the circuit  
b) Find the voltmeter reading

- 6.

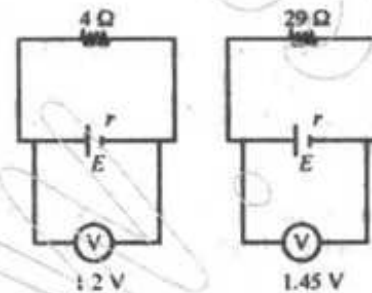

$$\mathcal{E} = 1.5 \text{ V}$$

$$r = 1 \Omega$$

Try first ya!

The diagram on the left shown that a cell is connected to a 4  $\Omega$  resistor and voltmeter reading is 1.2 V. Then the 4  $\Omega$  resistor is being substituted with a 29  $\Omega$  resistor and found that voltmeter reading becomes 1.45 V. Find the e.m.f and the internal resistance of the cell